

## حل التمرين 07

$$u = u_1 + u_2 \Rightarrow \boxed{u_2 = u - u_1} \Rightarrow u_2 = 4V$$

$$u - u_3 - u_4 - u_5 = 0 \Rightarrow \boxed{u_4 = u - u_3 - u_5} \Rightarrow u_4 = 4V$$

$$u_6 + u_7 + u_4 = 0 \Rightarrow \boxed{u_7 = -u_4 - u_6} \Rightarrow u_6 = 2V$$